Sessional II Total points	18/20	?
Email * shantanubobade1@gmail.com		
Enter Your Name * SHANTANU SANJAY BOBADE		
Enter Your Roll Number * 31		
X An arithmetic circuit that subtracts one binary digit from another considering a borrow is called a		0/2
Full adder		
Full Subtractor		
Half-Adder		×
O Half-Subtractor		
Correct answer		
Half-Subtractor		

 An arithmetic circuit that adds only two binary digits is called a 	2/2
half subtractor	
half adder	✓
adder	
o parallel adder	
✓ Which of the following logic circuit accepts two binary digits on inputs and produces two binary digits, a sum bit and a carry bit on its output	
Serial adder	
Parallel adder.	
Full Adder	
Half-adder	✓
✓ A full adder can be realized using	2/2
two half-adder, one OR gate	✓
two half-adder , two OR gates	
two half-adder , one AND gates	
one half-adder , two OR gates	

2/11/22, 11:36 AM Sessional II

✓ In digital systems subtraction is perfor	med 2/	2
Using half-adders		
Using half-subtractors		
Using adder with 1's complement represent	tation of negative numbers	
By None of the above.		
To secure a higher speed of addition, v preferred solution?	which of the following is the 2/3	2
Serial adder		
Parallel Adder		
Full-adder		
Adder with a look-ahead-carry	✓	
✓ How many inputs and outputs does a f	full-adder have? 2/	2
Two inputs, Three outputs		
Two inputs, two outputs		
Three inputs, two outputs	✓	
Two inputs, one output		

 A full-adder and a full-subtractor can be realized by using at least NAND gates. 	2/2
O 7	
<u> </u>	
O 10	
9	✓
✓ The difference output in a full – subtractor is the same as the	2/2
Difference output of a half-subtractor	
carry output of a full adder	
sum output of a full-adder	✓
sum output of a half-adder	
✓ How many full-adders are required to construct an m-bit parallel add	der? 2/2
m/2	
m-1	
o m	✓
m+1	

This content is neither created nor endorsed by Google. - <u>Terms of Service</u> - <u>Privacy Policy</u>

Google Forms

E